

---

## *Application Note*

---

# *Interfacing SRAM to EP7xxx Series Microcontrollers*



Note: Cirrus Logic assumes no responsibility for the attached information which is provided "AS IS" without warranty of any kind (expressed or implied).

---

### *Preliminary Product Information*

This document contains information for a new product.  
Cirrus Logic reserves the right to modify this product without notice.

---

## TABLE OF CONTENTS

|                                             |          |
|---------------------------------------------|----------|
| <b>1. INTRODUCTION .....</b>                | <b>3</b> |
| <b>2. GENERAL DISCUSSION .....</b>          | <b>3</b> |
| <b>3. DESIGN OF THE BYTE DECODERS .....</b> | <b>3</b> |
| 3.1 Decoding x16 SRAM .....                 | 4        |
| 3.2 Decoding x32 SRAM .....                 | 6        |
| <b>4. LISTING 1 SAMPLE PROGRAM .....</b>    | <b>9</b> |

## LIST OF FIGURES

|                                                                               |   |
|-------------------------------------------------------------------------------|---|
| Figure 1. Listing 1 Timing Diagram .....                                      | 4 |
| Figure 2. Schematic for Three Types of SRAM Interfaces (Landscape View) ..... | 5 |
| Figure 3. x32 SRAM Interface with Decoding of Four Byte Lanes .....           | 8 |

## LIST OF TABLES

|                                                   |   |
|---------------------------------------------------|---|
| Table 1. Truth Table for x16 Memory Accesses..... | 4 |
| Table 2. Truth Table for x32 Memory Accesses..... | 6 |
| Table 3. Karnaugh Graph #1.....                   | 6 |
| Table 4. Karnaugh Graph #2.....                   | 7 |
| Table 5. Karnaugh Graph #3.....                   | 7 |
| Table 6. Karnaugh Graph #4.....                   | 7 |

## Contacting Cirrus Logic Support

For a complete listing of Direct Sales, Distributor, and Sales Representative contacts, visit the Cirrus Logic web site at:  
<http://www.cirrus.com/corporate/contacts/>

Preliminary product information describes products which are in production, but for which full characterization data is not yet available. Advance product information describes products which are in development and subject to development changes. Cirrus Logic, Inc. has made best efforts to ensure that the information contained in this document is accurate and reliable. However, the information is subject to change without notice and is provided "AS IS" without warranty of any kind (express or implied). No responsibility is assumed by Cirrus Logic, Inc. for the use of this information, nor for infringements of patents or other rights of third parties. This document is the property of Cirrus Logic, Inc. and implies no license under patents, copyrights, trademarks, or trade secrets. No part of this publication may be copied, reproduced, stored in a retrieval system, or transmitted, in any form or by any means (electronic, mechanical, photographic, or otherwise) without the prior written consent of Cirrus Logic, Inc. Items from any Cirrus Logic web site or disk may be printed for use by the user. However, no part of the printout or electronic files may be copied, reproduced, stored in a retrieval system, or transmitted, in any form or by any means (electronic, mechanical, photographic, or otherwise) without the prior written consent of Cirrus Logic, Inc. Furthermore, no part of this publication may be used as a basis for manufacture or sale of any items without the prior written consent of Cirrus Logic, Inc. The names of products of Cirrus Logic, Inc. or other vendors and suppliers appearing in this document may be trademarks or service marks of their respective owners which may be registered in some jurisdictions. A list of Cirrus Logic, Inc. trademarks and service marks can be found at <http://www.cirrus.com>.

## 1. INTRODUCTION

This application note explains how to interface SRAM memory to the bus of Cirrus Logic ARM-based microcontrollers. The bus controller on these devices can interface to x8-, x16-, or x32-bit wide data memory. However, when using a x16 or x32 bus configurations, it requires some external decoding logic.

## 2. GENERAL DISCUSSION

The EP7xxx microcontrollers are capable of interfacing to a wide variety of SRAM memory devices. Extra SRAM may be required if the internal SRAM provided in the EP7xxx is insufficient for a particular application. SRAM can also be used to hold program memory. Since some SRAM devices can have fast access speeds, that can help to improve overall system performance. However, the ARM architecture does not support unaligned accesses, which means that accessing bytes on non-aligned addresses require an external decoder to access individual "byte-lanes". In most situations, external logic to decode the byte lanes may be required.

Three types of SRAM configurations are shown in [Figure 2](#). The first configuration is for x8 memory. In this case, no extra decoding logic is needed. For reading and storing 8-bit data, this scheme works well as each byte is accessed for each data access cycle, assuming a STRB or LDRB instruction is used (store byte or load byte). Furthermore, the byte data can be accessed on any byte-bounded memory location. When using x8 memory for program storage, the processor has to fetch 4 bytes to build up an instruction word (or two bytes in the case of a Thumb instruction) which can slow down performance by a factor of four.

The second SRAM memory bank example in [Figure 3](#) is a x16 SRAM with no byte decoding since both nUB and nLB (upper-byte and lower-byte) signals are tied low. This limits the processor from using byte data since it can only access data

on a half-word or on a 16-bit boundary. This means that the programmer must take care to cast all char data as half-word which pads the upper byte with don't cares thereby wasting half of available memory space. But it can also be dangerous, especially when using vendor provided libraries that expect data to be on byte-boundaries. Byte decoding of x16 SRAM may not be necessary when using SRAM to store instructions only. The reason is to take advantage of the faster access times of SRAM verses the slower memory access time of x16 Flash or EPROM. But it will still take two memory fetches for each ARM instruction (or one for Thumb).

It is possible to use x32 SRAM without byte decoding, but it is *not recommended*. In theory, one could use non-decoded x32 SRAM for storing instructions (for speed improvement). But in this case, Thumb instructions must be aligned on word boundaries which is impractical. If using this type of memory for data, then only 32-bit words can be reliably accessed.

In conclusion, it is generally recommended that when using x16 and x32 external SRAM, each byte lane be fully decoded.

## 3. DESIGN OF THE BYTE DECODERS

The program in Listing 1 (See "[Listing 1 Sample Program](#)") is designed to write 4 bytes, 4 half-ints, and 4 ints to a hypothetical memory device. Chip select #5 is used which gives a default address range starting at location 0x5000.0000 (this can be changed by the MMU). The results were sampled using a HP 16500B logic analyzer and is displayed in [Figure 1](#). The signals sampled are: A0 and A1 (address bits), nCS5 (chip select 5), nMOE (output enable), HALFWORD and WORD. From the waveforms, truth tables can be derived and logic synthesized.

The first four access are byte oriented, the next four are word (32-bit) oriented, and the last four are

 


Figure 1. Listing 1 Timing Diagram

half-word accesses. Each access is denoted by a negative signal on NCS5.

### 3.1 Decoding x16 SRAM

From Figure 1, it can be seen that a truth table as shown in Table 1 can be constructed to provide decoding of byte accesses. In this case, nLB and nUB are signals applied to a x16 SRAM to decode the lower and upper bytes, respectively.

By inspection and by applying DeMorgan's Theorem, the equations for a byte decoder are listed below:

$$\text{nLB} = \neg(W + HW + A0)$$

$$\text{nUP} = \neg(W + HW + A0)$$

The schematic in Figure 2 has logic that implements the equations above.

| ACCESS | WORD | HALF WORD | A0 | nLB | nUP |
|--------|------|-----------|----|-----|-----|
| Word   | 1    | X         | X  | 0   | 0   |
| Half   | 0    | 1         | X  | 0   | 0   |
| Byte   | 0    | 0         | 0  | 0   | 1   |
| Byte   | 0    | 0         | 1  | 1   | 0   |

Table 1. Truth Table for x16 Memory Accesses

 


Figure 2. Schematic for Three Types of SRAM Interfaces (Landscape View)

### 3.2 Decoding x32 SRAM

Typically, two x16 devices would be used to create a x32 SRAM memory block. In this case, A0 and A1 are used to decode the byte lanes along with HALFWORD and WORD. The truth table is listed below in [Table 2](#):

| Access     | WORD | HALFWORD | A0 | A1 | nB0 | nB1 | nB2 | nB3 |
|------------|------|----------|----|----|-----|-----|-----|-----|
| Word       | 1    | X        | X  | X  | 0   | 0   | 0   | 0   |
| Lower Half | 0    | 1        | X  | 0  | 0   | 0   | 1   | 1   |
| Upper Half | 0    | 1        | X  | 1  | 1   | 1   | 0   | 0   |
| Byte 0     | 0    | 0        | 0  | 0  | 0   | 1   | 1   | 1   |
| Byte 1     | 0    | 0        | 1  | 0  | 1   | 0   | 1   | 1   |
| Byte 2     | 0    | 0        | 0  | 1  | 1   | 1   | 0   | 1   |
| Byte 3     | 0    | 0        | 1  | 1  | 1   | 1   | 1   | 0   |

Table 2. Truth Table for x32 Memory Accesses

The logic to implement the byte decoding is more complicated, but can be easily realized using a low cost PAL or generic logic, such as a GAL16V8 or PAL16L8. The equations are derived using Karnaugh graphs. The equations are not fully reduced to minimum terms. The terms W and HW stand for WORD and HALFWORD, respectively. The schematic in [Figure 3](#) illustrates one method.

For nB0:

A0, A1

|       |    | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|----|
| W, HW | 00 | 0  | 1  | 1  | 1  |
|       | 01 | 0  | 1  | 1  | 0  |
|       | 11 | 0  | 0  | 0  | 0  |
|       | 10 | 0  | 0  | 0  | 0  |

Table 3. Karnaugh Graph #!

$$nB0 = (!W * A1) + (!W * !HW * A0)$$

For nB1:

|       |    |        |    |    |    |
|-------|----|--------|----|----|----|
|       |    | A0, A1 |    |    |    |
|       |    | 00     | 01 | 11 | 10 |
| W, HW | 00 | 1      | 0  | 1  | 1  |
|       | 01 | 0      | 1  | 1  | 0  |
|       | 11 | 0      | 0  | 0  | 0  |
|       | 10 | 0      | 0  | 0  | 0  |

**Table 4. Karnaugh Graph #2**

$$nB1 = (!W * HW * !A0) + (!W * !HW * A0) + (!W * !HW * !A1)$$

For nB2:

|       |    |        |    |    |    |
|-------|----|--------|----|----|----|
|       |    | A0, A1 |    |    |    |
|       |    | 00     | 01 | 11 | 10 |
| W, HW | 00 | 1      | 1  | 1  | 0  |
|       | 01 | 1      | 0  | 0  | 1  |
|       | 11 | 0      | 0  | 0  | 0  |
|       | 10 | 0      | 0  | 0  | 0  |

**Table 5. Karnaugh Graph #3**


$$nB2 = (!W * HW * !A1) + (!W * !HW * A0) + (!W * !HW * A1)$$

For nB3:

|       |    |        |    |    |    |
|-------|----|--------|----|----|----|
|       |    | A0, A1 |    |    |    |
|       |    | 00     | 01 | 11 | 10 |
| W, HW | 00 | 1      | 1  | 0  | 1  |
|       | 01 | 1      | 0  | 0  | 1  |
|       | 11 | 0      | 0  | 0  | 0  |
|       | 10 | 0      | 0  | 0  | 0  |

**Table 6. Karnaugh Graph #4**

$$nB3 = (!W * !HW * !A0) + (!W * !A1)$$

 

**Figure 3. x32 SRAM Interface with Decoding of Four Byte Lanes**

## 4. LISTING 1 SAMPLE PROGRAM

The program set out below in this section was used to read 8, 32, and 16-bit data from the EP72xx. The timing diagram on shown in [Figure 1](#) is a print out from a logic analyzer showing the results.

```
//byte, int, and half word access program
#define byte unsigned char
int
main(void)
{
    byte * mem;
    int * mem32;
    byte a,b,c,d;
    int e,f,g,h;
    short * mem16;
    short i,j,k,l;
    while(1)
    {
        //Set start address to 0x5000.0000 and read four bytes
        mem = (byte*) 0x50000000;
        a=*mem;
        mem++;
        b=*mem;
        mem++;
        c=*mem;
        mem++;
        d=*mem;
        //Next, reset 32 bit pointer and read in four words
        mem32 = (int*) 0x50000000;
        e=*mem32;
        mem32++;
        f=*mem32;
        mem32++;
        g=*mem32;
        mem32++;
        h=*mem32;
        //Finally, define a 16-bit pointer and read in four half-words
        (short)
        mem16 = (short *) 0x50000000;
        i=*mem16;
        mem16++;
        j=*mem16;
        mem16++;
        k=*mem16;
        mem16++;
        l=*mem16;
    }
}
```

