Isolated Products


SLTA020A

(Revised 6/30/2000)

Using the PT4200/4205/4300 DC to DC Converter


Remote Control (RC) Turn-on or turn-off can be realized by using the RC pin. Normal operation is achieved if pin 11 is open. If pin 11 is connected to pin 17 (PT4200/4300) or pin 18 (PT4205), the power module turns off. To insure safe turn-off, the voltage difference between pin 11 and 17 or 18 should be less than 1.0V. RC is compatible with TTL open collector outputs with a sink capacity > 300μ A (see figure 28).

Figure 28
PT4200/4205/4300 REMOTE CONTROL

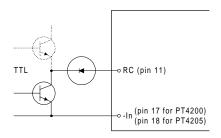

Over Voltage Protection (OVP) The remote control can also be utilized for OVP by using the external circuitry shown in figure 29. Resistor values are for 5V output applications, but can easily be adjusted for other output voltages and the desired OVP level.

Figure 29
PT4200/4205/4300 OVER VOLTAGE PROTECTION

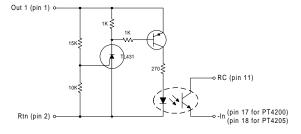

Turn-on/off Input Voltage The power module monitors the input voltage and will turn on and turn off at predetermined levels set by means of external resistors.


To increase V_{Ion} connect a resistor between pin 11 and 17 (PT4200/4300) or 18 (PT4205) (see figure 30). The resistance is determined by the following equations; (a) PT4200/4300, (b) PT4205:

(a) R_{lon} = 100 x (100.2 - V_{lon})/(V_{lon} - 36.5) k Ω (for V_{lon} >37V) (b) R_{lon} = 1000 x (1110 - V_{lon})/(V_{lon} - 18.7) k Ω (for V_{lon} >18.7V) where 18.7 or 36.5 is the typical unadjusted turn-on input voltage. V_{loff} is the adjusted turn-off input voltage and is determined by V_{lon} - V_{loff} = 2V (typical value).

To decrease V_{Ion} connect a resistor between pin 10 and 11 (see figure 30). The resistance is determined by the following equations; (a) PT4200/4300, (b) PT4205:

- (a) $R_{Ion} = 364 \text{ x} (V_{Ion} 29.9)/(36.5 V_{Ion}) \text{ k}\Omega \text{ (for 30 < V}_{Ion} < 36 \text{V)}$
- (b) $R_{Ion} = 25 \text{ x} (V_{Ion} 16.9)/(18.7 V_{Ion}) \text{k}\Omega$ (for 16.9< $V_{Ion} < 18.7 \text{ V}$)

Figure 30
PT4200/4205/4300 TURN-ON/OFF INPUT VOLTAGE ADJUSTMENT

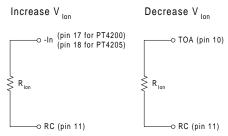

Ouput Voltage Adjust (Vadj) Ouput voltage can be adjusted by using an external resistor. Typical adjust range is $\pm 15\%$. If pin 8 and 9 are not connected together, the output will decrease to a low value. To increase V_o , a resistor should be connected between pin 8/9 and 18. To decrease V_o , a resistor should be connected between pin 8 and 9 (see figure 31).


The typical resistor value to **increase** V_0 is determined by:

The typical resistor value to **decrease** V_o is determined by:

	$R_{adj} = k_1 \times (V_{Oi} - V_{O}) / (V_{O} - k_2) \times \Omega$		
where	$k_1 = 2.751$	$k_{2}=1.75V$	PT4201
	$k_1 = 1.986$	$k_2 = 2.59V$	PT4202
	$k_1 = 1.986$	k,=4.12V	PT4203
	$k_1 = 2.284$	k,=9.52V	PT4204
	$k_1 = 17.2$	$k_{5}=1.70V$	PT4205
	$k_1 = 12.5$	k,=4.28V	PT4206
	$k_1 = 1.986$	k,=4.12V	PT4301
	$k_1 = 1.986$	k,=2.59V	PT4302
	$k_1 = 2.284$	$k_2 = 9.52V$	PT4303

* Over 13.8V output voltage, the input voltage range is limited to 38-65V.

Figure 31
PT4200/4205/4300 OUTPUT VOLTAGE ADJUSTMENT

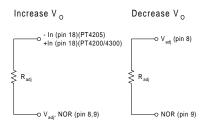



IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgment, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

Customers are responsible for their applications using TI components.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.

Copyright © 2000, Texas Instruments Incorporated