


S3033

Board Decoupling Guidelines

SONET/SDH/ATM OC-3/12 Transceiver S3033 Example

The S3033 transceiver chip is a fully integrated serialization/deserialization SONET OC-12 (622.08 Mbit/s) and OC-3 (155.52 Mbit/s) interface device. Figure 1 illustrates the connections for the S3033 device. External capacitors are required for power supply decoupling only. The inductor is a Murrata BLM31B601SPB or BLM11B601SPB surface mount ferrite. The double capacitors shown are parallel 0.1 μ F X7R and 100 pF are COG or NPO ceramic chip. The CAP1/CAP2 capacitor should be 0.01 μ F X7R. Note that the 0.1 μ F should be placed on the bottom side of the board for better capacitor efficiency. The Low ESR 10 μ F capacitor and 0 Ω resistor are optional for AVCC, for higher noise environments.

Figure 1. S3033 Connections

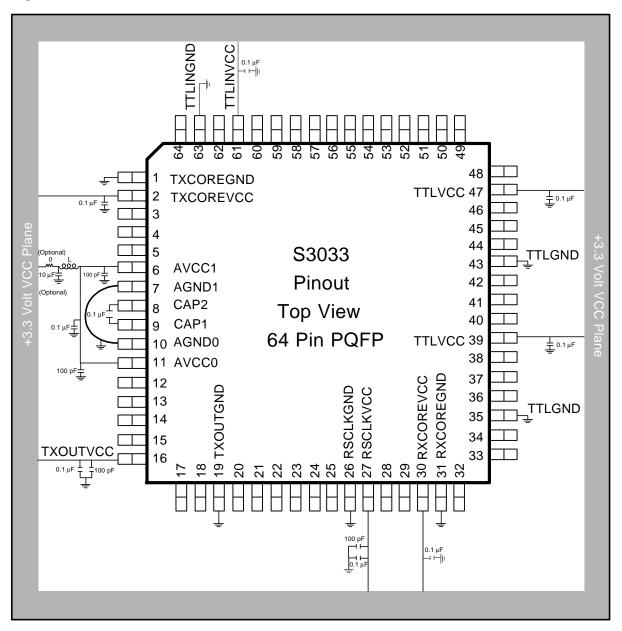



Applied Micro Circuits Corporation 6290 Sequence Dr., San Diego, CA 92121

Phone: (858) 450-9333 — (800) 755-2622 — Fax: (858) 450-9885

http://www.amcc.com

AMCC reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

AMCC does not assume any liability arising out of the application or use of any product or circuit described herein, neither does it convey any license under its patent rights nor the rights of others.

AMCC reserves the right to ship devices of higher grade in place of those of lower grade.

AMCC SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS.

AMCC is a registered trademark of Applied Micro Circuits Corporation. Copyright © 2000 Applied Micro Circuits Corporation.