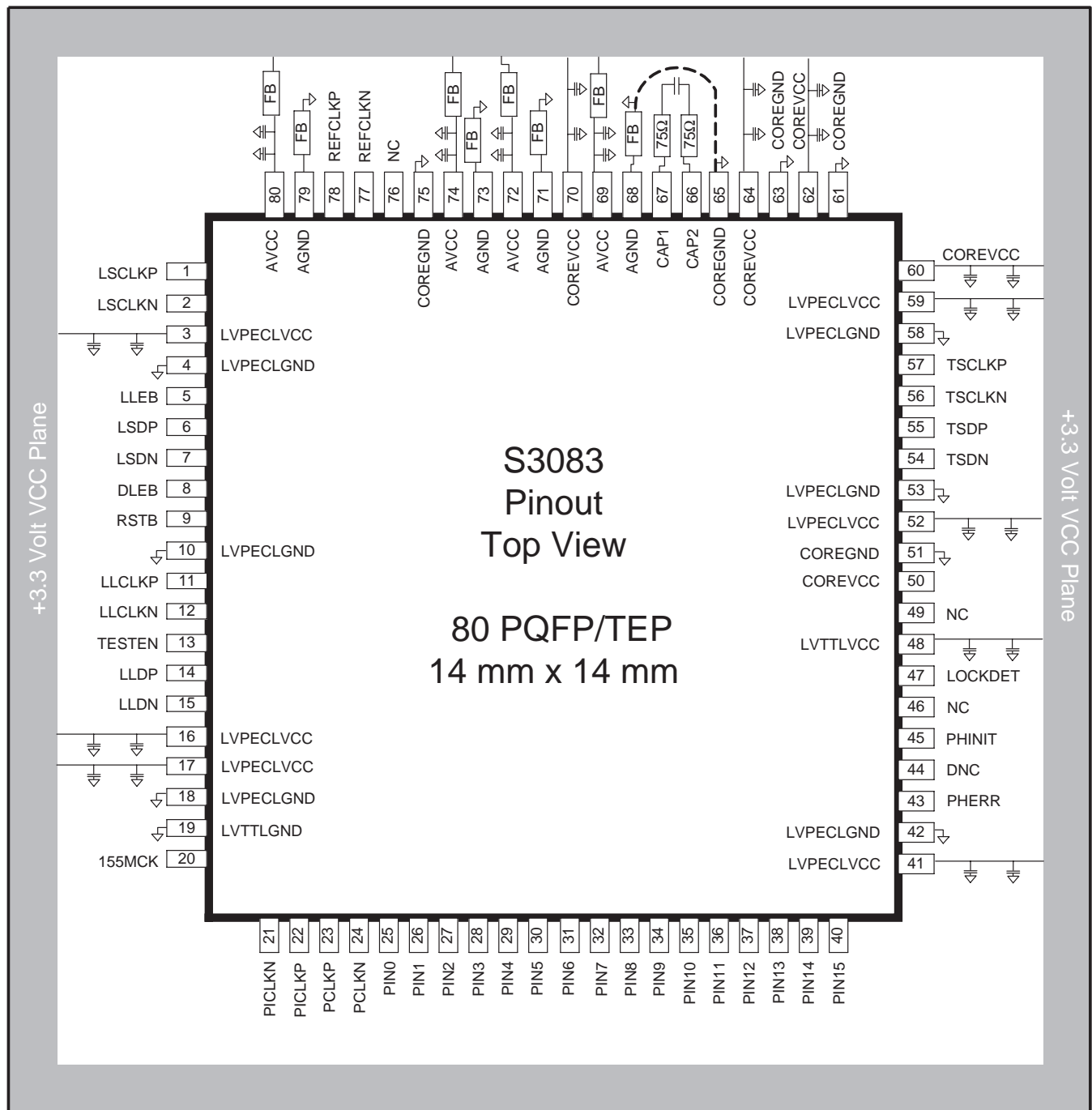


SONET/SDH/ATM S3083 EXAMPLE

The S3083 transmitter performs parallel-to-serial conversion for OC-48/STM-16 2.488 Gbit/s NRZ data. The CAP1/CAP2 capacitor should be 2.2μF. The figure below illustrates the decoupling connections for the S3083 device. The ground ring is shown around the loop filter capacitor. Please note that the ring should be directly connected to the ground plane to avoid current through the ground ring. The values of the decoupling components are 0.1μF paralleled with 100pF, X7R dielectric, EIA sizes 0603 and 0805. Ferrite Bead Inductors are murata BLM31B601S or equivalent. All grounds must be tied directly to ground plane. (Note: Do not daisy chain grounds together.) AGND/GND should be tied to ground directly or via ferrites as shown.





Applied Micro Circuits Corporation • 6290 Sequence Dr., San Diego, CA 92121

Phone: (858) 450-9333 • (800) 755-2622 • Fax: (858) 450-9885

<http://www.amcc.com>

AMCC reserves the right to make changes to its products or to discontinue any semiconductor product or service without notice, and advises its customers to obtain the latest version of relevant information to verify, before placing orders, that the information being relied on is current.

AMCC does not assume any liability arising out of the application or use of any product or circuit described herein, neither does it convey any license under its patent rights nor the rights of others.

AMCC reserves the right to ship devices of higher grade in place of those of lower grade.

AMCC SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, INTENDED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT APPLICATIONS, DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS.

AMCC is a registered trademark of Applied Micro Circuits Corporation.
Copyright © 1999 Applied Micro Circuits Corporation