

1. General

The filter is symmetrical, i.e. input and output are exchangeable with each other. But the external coupling coil has to be connected to pin 3 in any case.

The filter can be driven balanced only.

To get a balanced signal for test measurements with the network analyzer we use two wideband 1:1 transformers at each port:

SMT 4, vendor NEOSID, PN 88 8529 10

The calibration for the plots was made at the 50 Ohm ports. Thus, the measured characteristics include the losses of the two transformers (about 0.7 dB each).

The termination impedances are : **580 Ω || -0.72 pF**

This impedance is equal for the input and the output. It has to be realized at the point where the filter is mounted. To match this impedance to the impedance of the system a matching circuit is required.

2. Theoretical matching


For the matching of termination impedances to 50 Ohm there can be used two different matching circuits:

50 Ohm test circuit 1

VI TELEFILTER
Potsdamer Straße 18
D 14 513 TELTOW / Germany
Tel: (+49) 3328 4784-0 / Fax: (+49) 3328 4784-30
0075
E-Mail: tft@telefilter.com


Vectron International, Inc.
267 Lowell Road
Hudson, NH 03051 / USA
Tel: (603) 598-0070 Fax: (603) 598-
E-Mail: vti@vtinh.com

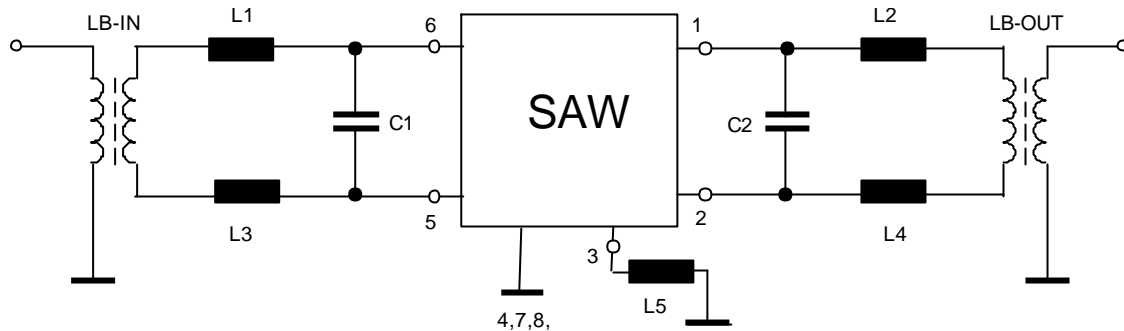VI TELEFILTER reserves the right to make changes to the product(s) and/or information contained herein without notice. No liability is assumed as a result of their use or application. No rights under any patent accompany the sale of any such product(s) or information.



$L1 = L2 = L3 = L4 = 32.39 \text{ nH}$
 $C1 = C2 = 1.51 \text{ pF}$
 $L5 = 47 \text{ nH}$

50 Ohm test circuit 2

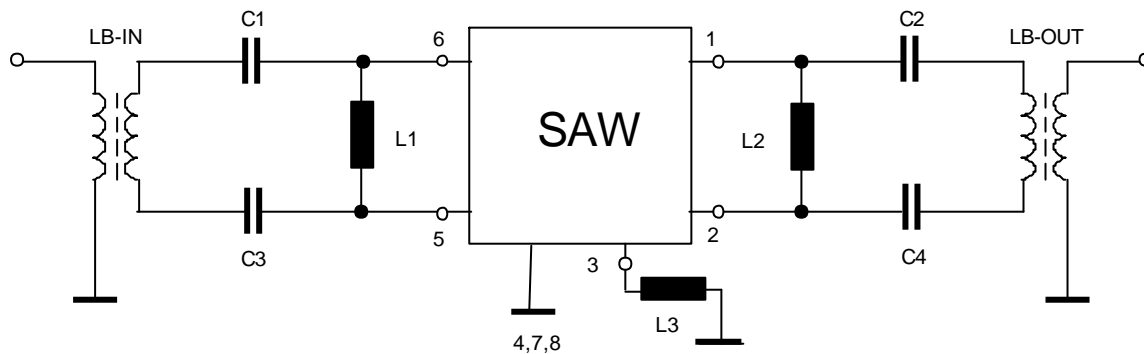

$C1 = C2 = C3 = C4 = 4.88 \text{ pF}$
 $L1 = L2 = 53.60 \text{ nH}$
 $L5 = 47 \text{ nH}$

3. Matching on PCB

VI TELEFILTER
Potsdamer Straße 18
D 14 513 TELTOW / Germany
Tel: (+49) 3328 4784-0 / Fax: (+49) 3328 4784-30
0075
E-Mail: tft@telefilter.com

Vectron International, Inc.
267 Lowell Road
Hudson, NH 03051 / USA
Tel: (603) 598-0070 Fax: (603) 598-
E-Mail: vti@vtinh.com

VI TELEFILTER reserves the right to make changes to the product(s) and/or information contained herein without notice. No liability is assumed as a result of their use or application. No rights under any patent accompany the sale of any such product(s) or information.

VI TELEFILTER

Application Note

TFS 400B

3/2

The theoretical matching was done without consideration of parasitics. The elements which have to be used on the PCB are slightly different from the stated above.

For example: PCB with 50 Ω test circuit 1

L1 = 33 nH

L2 = L3 = 39 nH

L4 = 47 nH

C1 = 0.5 pF

C2 can be left

L5 = 56 nH

If requested we can supply with such a PCB and the measured S-parameters.

VI TELEFILTER
Potsdamer Straße 18
D 14 513 TELTOW / Germany
Tel: (+49) 3328 4784-0 / Fax: (+49) 3328 4784-30
0075
E-Mail: tft@telefilter.com

Vectron International, Inc.
267 Lowell Road
Hudson, NH 03051 / USA
Tel: (603) 598-0070 Fax: (603) 598-
0075
E-Mail: vti@vtinh.com

VI TELEFILTER reserves the right to make changes to the product(s) and/or information contained herein without notice. No liability is assumed as a result of their use or application. No rights under any patent accompany the sale of any such product(s) or information.