

**UC3842A FAMILY
FREQUENCY FOLDBACK TECHNIQUE PROVIDES PROTECTION**

Excessive power dissipation in switching devices can occur during start-up and overload conditions in many switchmode power supplies. Many sophisticated PWM controllers provide the means for protection against these conditions; however, simple low-cost controllers will require additional circuitry. The circuit described below utilizes only one additional resistor and transistor to enhance the performance of the UC3842A family of controllers.



The power supply output voltage is fed to the error amplifier inverting input (pin 2) at a 2.5 volt amplitude under normal operating conditions. During start-up or overload,

however, this voltage can drop to zero. The circuit shown uses this feedback voltage to divert normal charging current from the IC's timing capacitor to ground whenever the feedback voltage is below the 2.5 volt nominal. A linear three-to-one reduction of oscillator frequency is obtainable for most applications. This technique lengthens the potential maximum on-time and reduces the programmed deadtime. In many circuits, however, the peak current limit threshold is reached early in the cycle under these overload conditions, and this is not a problem. For most applications, the foldback resistor value (R_F) should equal that of the timing resistor (R_T).

EXAMPLE:

100 kHz operation, $R_T = 15k$, $C_T = 1$ nF, $R_F = 15k$, $Q_1 = 2N2907A$

OPERATING MODE	NORMAL	OVERLOAD
$V_{E/A}$ - (pin 2)	2.50V	0.00V
Oscillator Freq.	105 kHz	36 kHz

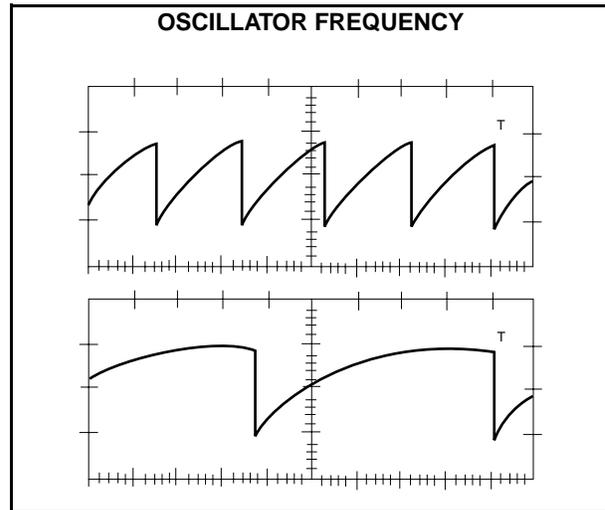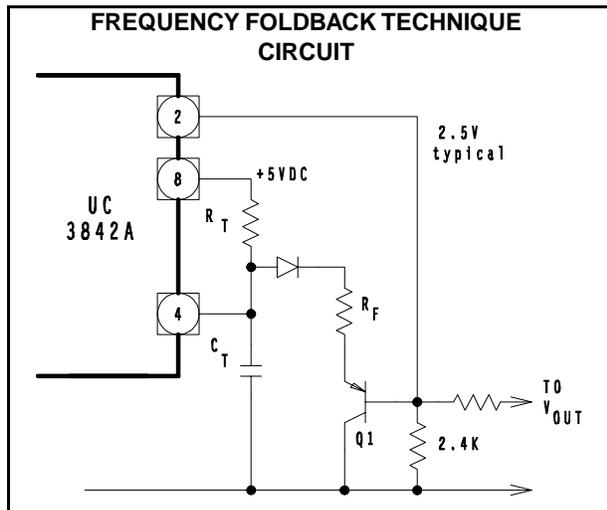

IMPORTANT NOTICE

Texas Instruments and its subsidiaries (TI) reserve the right to make changes to their products or to discontinue any product or service without notice, and advise customers to obtain the latest version of relevant information to verify, before placing orders, that information being relied on is current and complete. All products are sold subject to the terms and conditions of sale supplied at the time of order acknowledgement, including those pertaining to warranty, patent infringement, and limitation of liability.

TI warrants performance of its semiconductor products to the specifications applicable at the time of sale in accordance with TI's standard warranty. Testing and other quality control techniques are utilized to the extent TI deems necessary to support this warranty. Specific testing of all parameters of each device is not necessarily performed, except those mandated by government requirements.

CERTAIN APPLICATIONS USING SEMICONDUCTOR PRODUCTS MAY INVOLVE POTENTIAL RISKS OF DEATH, PERSONAL INJURY, OR SEVERE PROPERTY OR ENVIRONMENTAL DAMAGE ("CRITICAL APPLICATIONS"). TI SEMICONDUCTOR PRODUCTS ARE NOT DESIGNED, AUTHORIZED, OR WARRANTED TO BE SUITABLE FOR USE IN LIFE-SUPPORT DEVICES OR SYSTEMS OR OTHER CRITICAL APPLICATIONS. INCLUSION OF TI PRODUCTS IN SUCH APPLICATIONS IS UNDERSTOOD TO BE FULLY AT THE CUSTOMER'S RISK.

In order to minimize risks associated with the customer's applications, adequate design and operating safeguards must be provided by the customer to minimize inherent or procedural hazards.

TI assumes no liability for applications assistance or customer product design. TI does not warrant or represent that any license, either express or implied, is granted under any patent right, copyright, mask work right, or other intellectual property right of TI covering or relating to any combination, machine, or process in which such semiconductor products or services might be or are used. TI's publication of information regarding any third party's products or services does not constitute TI's approval, warranty or endorsement thereof.